******-------------------------*******

! An AoA Production... !

! ^ !

! !

! " Handy Telephone Circuits " !

! By: Eye-No Phonez !

! !

! With Excerpts from: !

! " Phone Color Boxes " !

/ Try These Psychadelic Boards : \

! !

! StoneHenge BBS 516-543-7995!

! Skull Island 3OOB 201-379-1459!

! Crooked Cops 515-225-8795!

! The Logic Center 515-223-4919!

_____/

Circuit #1:

Black Box with PushButton and
MouthPeice Amp...

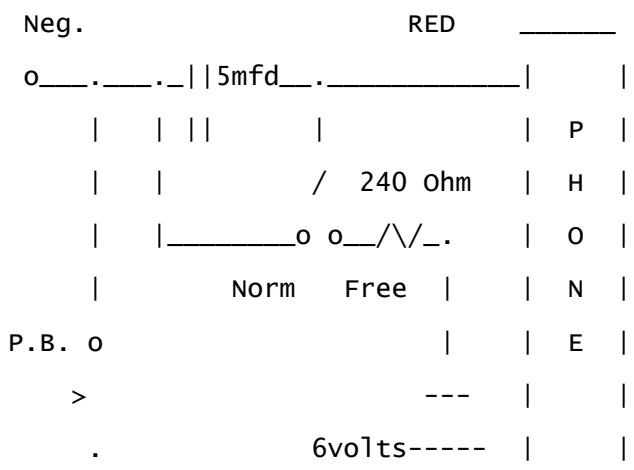

This diagram can be interpreted as:

P.B = Pushbutton
The 6 volt battery can be replaced with either a 9 or 12 volt battery, if you do so, you must also change the resistor value to the following:

Batt	Res. Value
6v	240
9v	360
12v	480

Make sure you don't use this on operator orignated calls. Otherwise this particular box plan is VERY VERY safe. When using it, after you answer the party will never know you are there, so you can screen calls that way .. work out a code with your friends who you'll allow to be Black Boxed, make it so they whistle while it is ringing or something so you know it's safe when you pick up to hit the pushbutton to kill the ringing. This is very important, if you DON'T hear the signal, DON'T black box that call! You can be nabbed if you mess up.

Circuit #2:

Put-Person-On-Hold

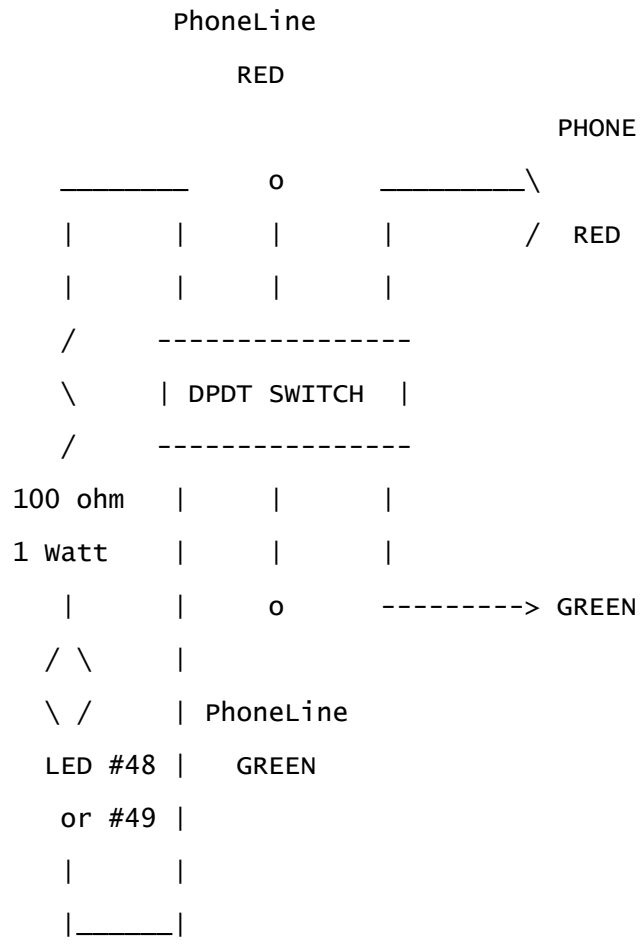

To activate Hold, switch DPDT.
LED will be on when Hold is on, and
off when it is off.

Here is a variation of the above
schmatic, this facilitates the use
of music to the person on hold:

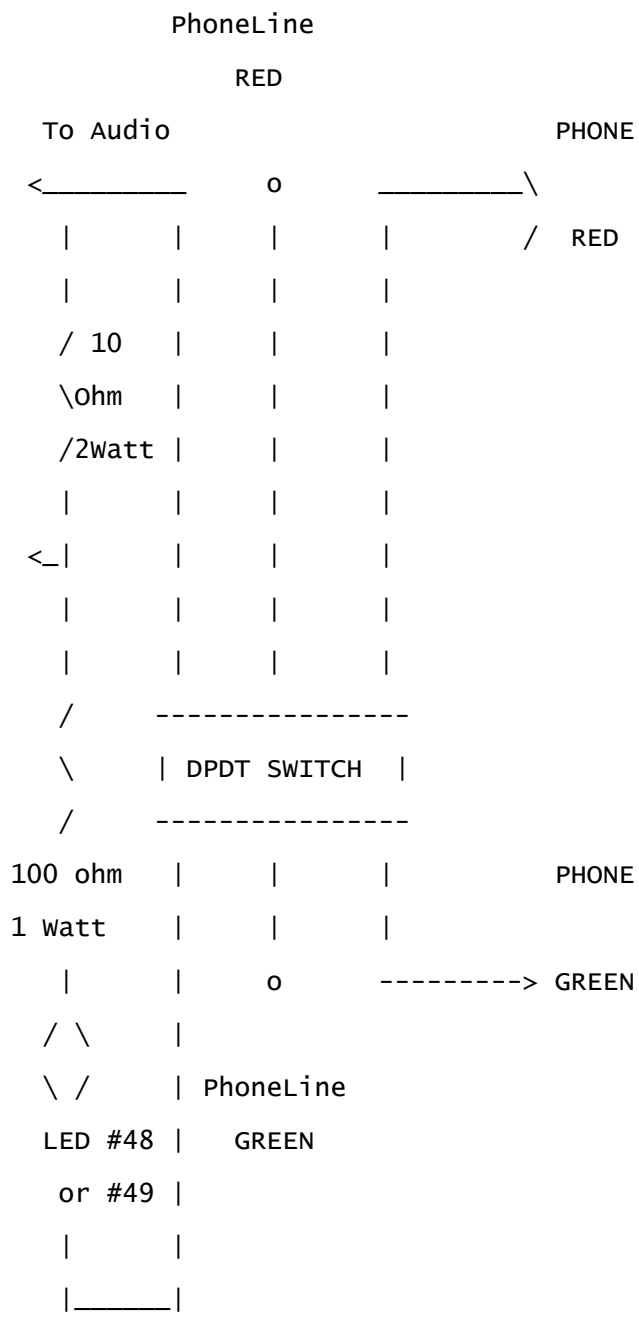

Circuit #3:

Snoop Lite (Tap/Bug Detector)

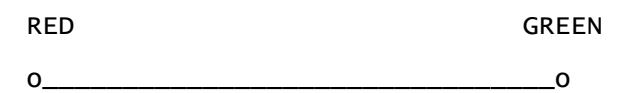

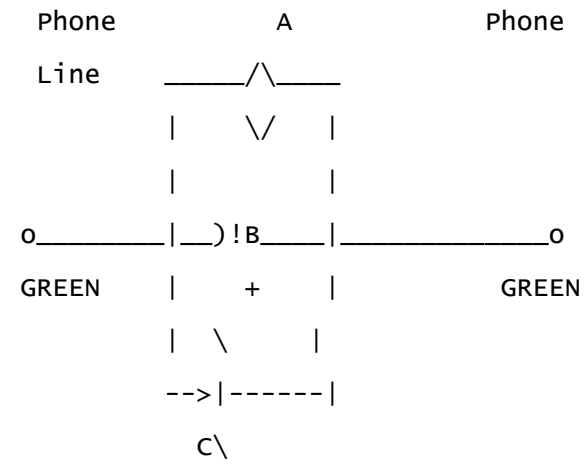

A - LED #48, OR #49

B - 500 MFD/15 VOLTS

C - 10 VOLT ZENER DIODE,1 WATT

LED will shine brightly when Tap or Bug or Extension is lifted.

******** Look for more in '87 ********

Disclaimer:

This file is produced for informational purposes only. It is not condoned, or practiced by the author. In no way should this be practiced. It is illegal.

This File is in accordance with The First Amendment of the Constitution of the United States Of America.